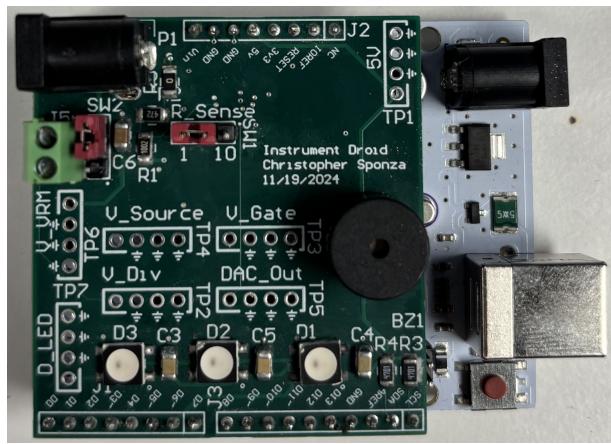


ECEN 3730 Board 4: Instrument Droid Shield

Christopher Sponza

December 4, 2024



1 Introduction

The purpose of the board was to create an Arduino shield that could take inputs from various voltage sources and characterize their Thevenin resistances and voltages at various currents.

Understanding the Thevenin equivalent circuit is a fundamental aspect of circuit design and analysis. By determining V_{th} and R_{th} engineers can gain better insight as to the response of a power source to varying loads, allowing for more accurate assessment of power stability and efficiency.

Although it was not necessary, this board was designed with 4-layers to serve as practice for working with multiple signal planes as well as mounting of parts on both sides of a PCB.

2 Plan of Record

2.1 “Back of Napkin” Sketch

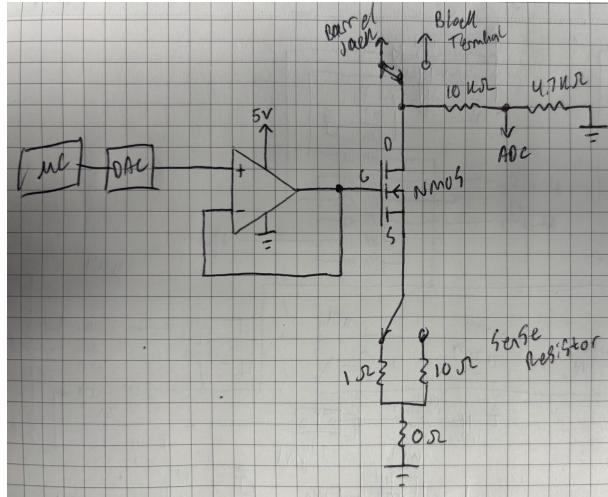


Figure 1: “Back of Napkin” Sketch

2.2 Description of the Circuit

Power is supplied via a barrel jack or block terminal to the drain of an NMOS. The voltage is divided with a $\frac{1}{3}$ divider using $10k\Omega$ and $5k\Omega$ resistors to meet the voltage requirements of the ADC. Using a digital signal from an Arduino the DAC sets the voltage at the gate of the NMOS to ensure a known current

through the sense resistor. The resolution of the measurement can be changed by selecting either the 1Ω or 10Ω sense resistor.

2.3 Engineering Specifications

The following were the specifications that were required to be met in order for the board to “work”:

- Have the option to have power supplied by a barrel jack or stripped leads at a block terminal with a 3-header selection switch.
- Mount directly on an Arduino Uno via header pins.
- Be able to characterize voltage sources both with a 10Ω and 1Ω sense resistor.
- Provide test points for:
 - The voltage of the source at the barrel jack or block terminal
 - V_{out} of the DAC
 - Voltage of the voltage divider
 - Source and Gate voltage of the MOSFET
 - 5V supply to the DAC, ADC, and Op-Amp
- Provide indication of measurement status with smart LEDs and a piezo speaker

2.4 Bill of Materials

Part	Value	Quantity
ADS1115 (ADS)	-	1
MCP6002T (Op-Amp)	-	1
U_MCP4725 (DAC)	-	1
AO3400A (NMOS)	-	1
Resistor	0Ω	2
-	1Ω	1
-	10Ω	1
-	4.7KΩ	3
-	10KΩ	1
Capacitor	1μF	3
-	22μF	3
Smart LED	-	3
Piezo Speaker	-	1
Position Header Connector	6 Pin	1
-	8 Pin	1
-	10 Pin	1
10x Probe TP	-	7
Power Jack (Barrel)	-	1
Power Jack (Block Terminal)	-	1
3-Pin Header (Switch)	-	2

2.5 Datasheets

- [MCP6002T: Op-Amp Datasheet](#)
- [ADS1115: ADS Datasheet](#)
- [U_MCP4725: DAC Datasheet](#)
- [AO3400A: NMOS Datasheet](#)

2.6 Milestones

The following are the main design milestones to reach the final product in chronological order:

- Define the engineering specifications
- Complete schematic and PCB design in Altium
- Critical Design Review (CDR)
- Board Assembly and Bring-Up
- Testing and accumulation of results

2.7 Testing Plan

- Apply 9V to the board via the barrel jack and verify expected voltage at the drain of the MOSFET and voltage divider. Do the same for the block terminal.
- Mount the board on a commercial Arduino and verify the smart LEDs and Piezo speaker can be properly controlled.
- Upload code to control the voltage output of the DAC and perform verification measurement at the DAC output and the source of the MOSFET to ensure it is turning on properly.
- Perform Thevenin measurements as follows:
 - Using a max current of 250mA, increment the voltage output of the DAC over 20 divisions at a 10% duty cycle to prevent over-heating of the MOSFET.
 - Measure the voltage at the divider as fast as possible with the ADS and average the result with the DAC both on and off.
 - At the end of each power cycle of the MOSFET the voltage measured while the DAC is off will be V_{th} . This value will be used with the DAC on voltage to calculate the R_{th} .
- Repeat the measurement process for a 5V power supply.

2.8 Final Product

The following schematic and PCB were designed in Altium:

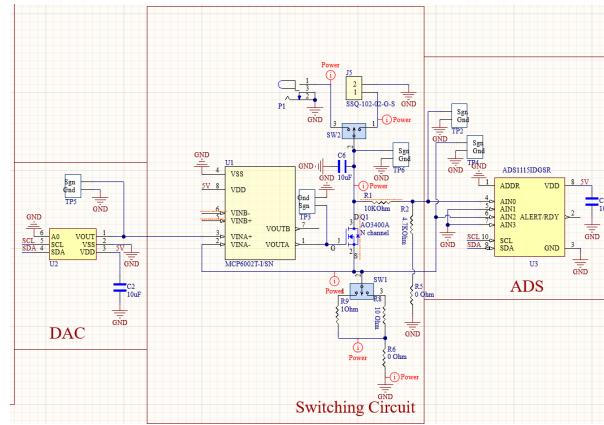


Figure 2: Data Collection Section of Schematic

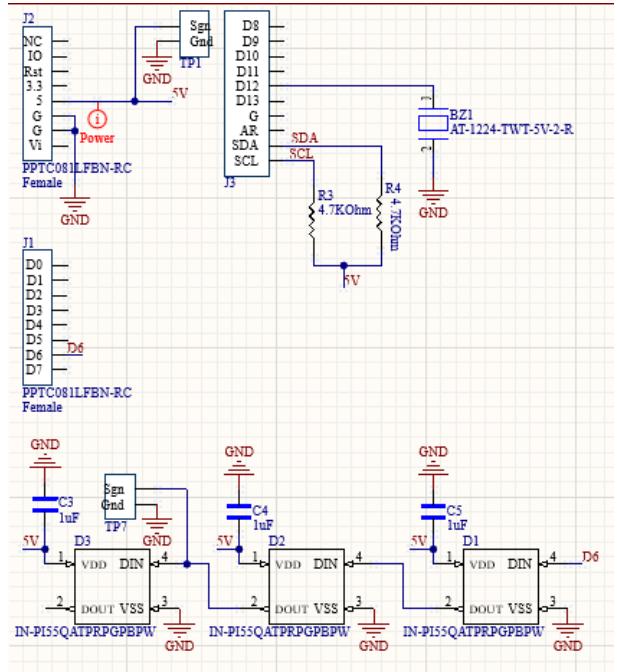


Figure 3: Smart LED and Header Pin Section of Schematic

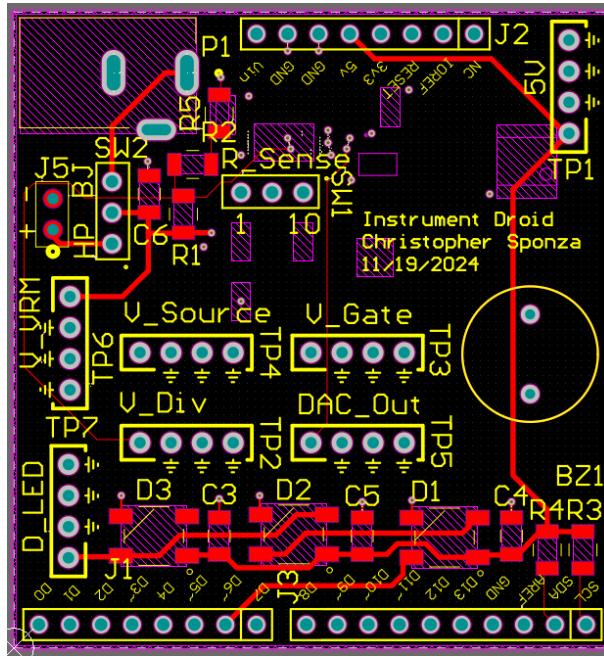


Figure 4: Board Designed in Altium (Top Signal Layer)

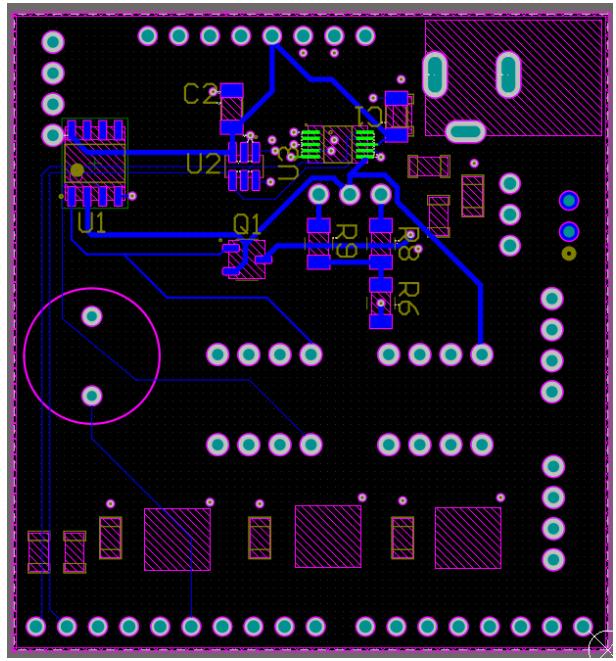


Figure 5: Board Designed in Altium (Bottom Signal Layer)

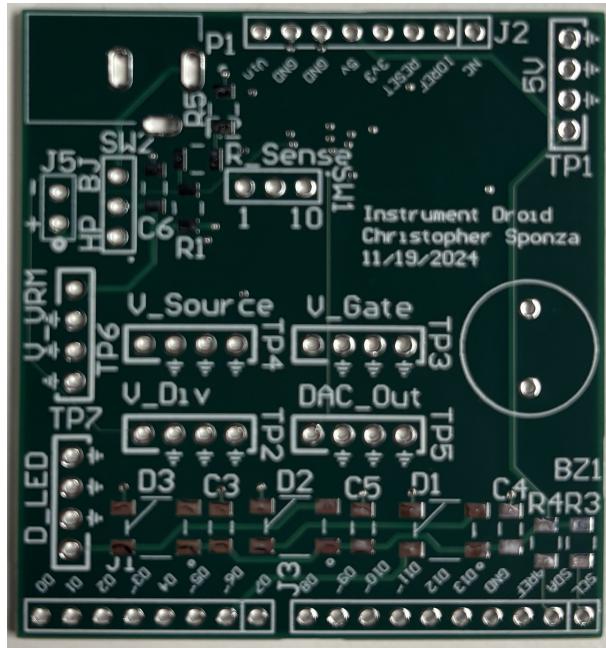


Figure 6: Board Received From the Manufacturer

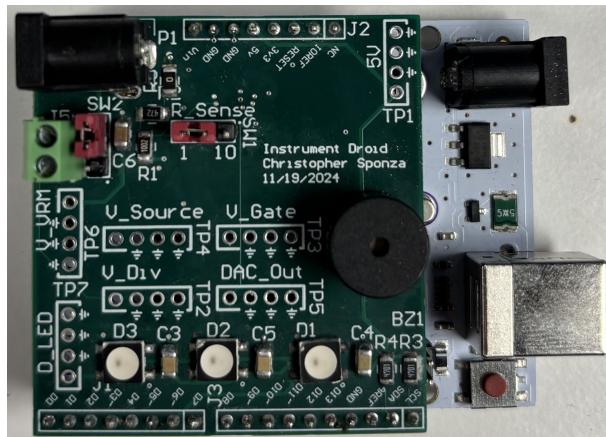


Figure 7: Constructed Board Mounted on Arduino Uno (Top)

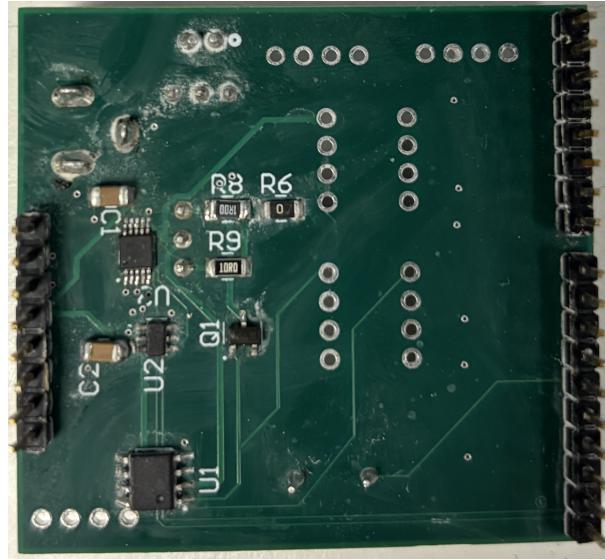


Figure 8: Constructed Board (Bottom)

3 Project Analysis and Measurement

3.1 Testing

3.1.1 Supply Voltage and Voltage Divider

I first supplied 9V to both the barrel jack and block terminal and verified expected voltages at the MOSFET drain and voltage divider.

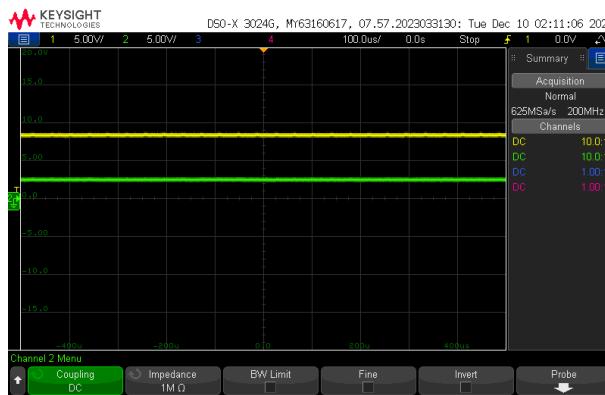


Figure 9: Oscilloscope Measurement at the drain of the MOSFET (Yellow) and Voltage Divider (Green) with 9V Supply at the Barrel Jack

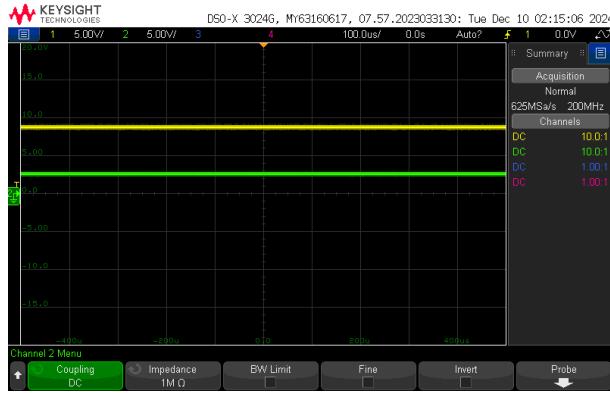


Figure 10: Oscilloscope Measurement at the drain of the MOSFET (Yellow) and Voltage Divider (Green) with 9V Supply at the Block Terminal

As can be seen in Figures 9 and 10 9V is properly received in both cases and there is roughly 3V at the voltage divider verifying the expected $\frac{1}{3}$ voltage division.

3.1.2 Smart LED Functionality

I next uploaded the code from Appendix A to perform the remainder of the testing including the control of the buzzer and smart LEDs, DAC output and ADC measurements, and Thevenin measurements.

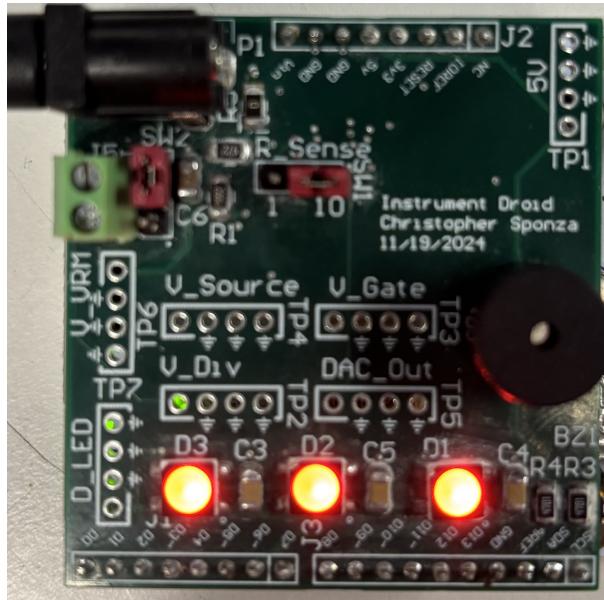


Figure 11: Smart LEDs at Beginning of Measurement Cycle

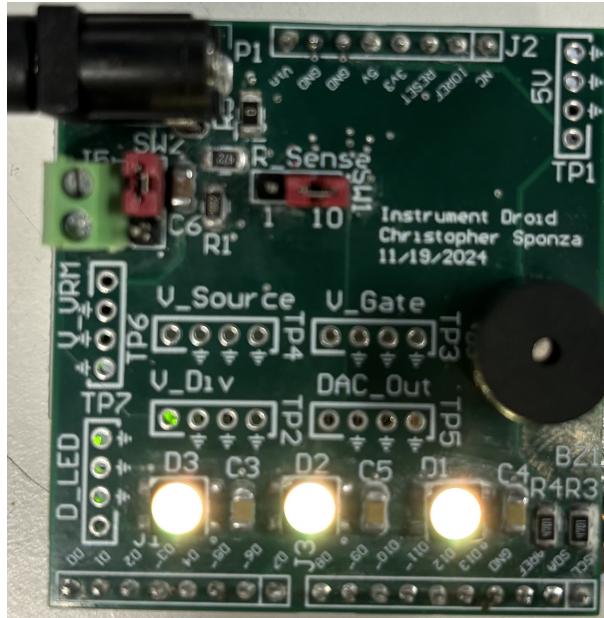


Figure 12: Smart LEDs in the Middle of Measurement Cycle

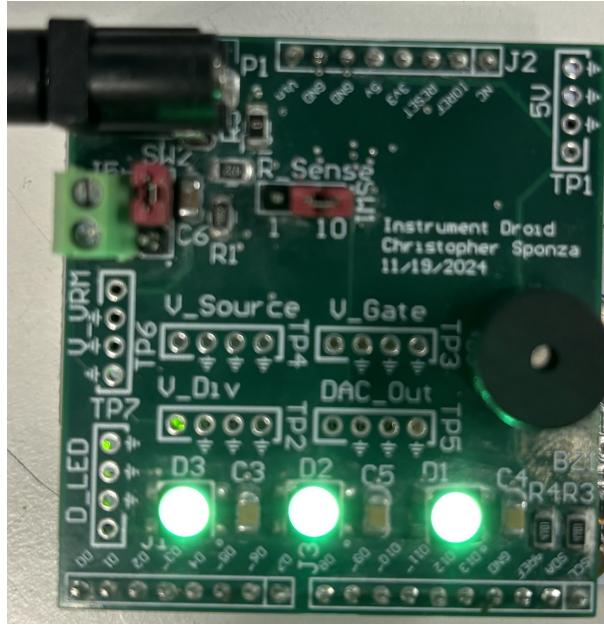


Figure 13: Smart LEDs at the end of the Measurement Cycle

Figures 11, 12, and 13 display the smart LED functionality through the beginning middle and end of the measurement cycle. Each time a measurement is taken the LEDs make an incremental change from red to green. At the completion of the measurement cycle the buzzer sounds as an indication.

3.1.3 DAC and ADC Verification

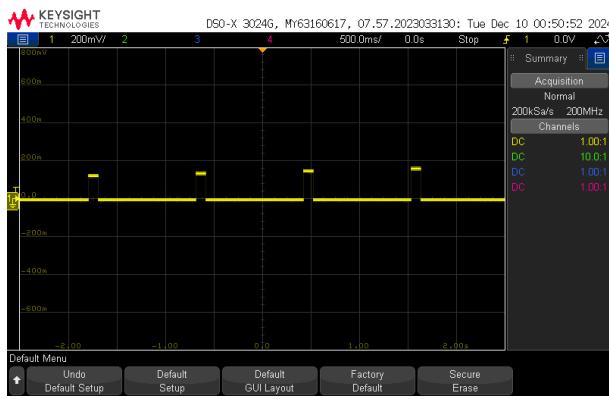


Figure 14: Output of the DAC Midway Through Measurement Cycle with 12.5mV Increments

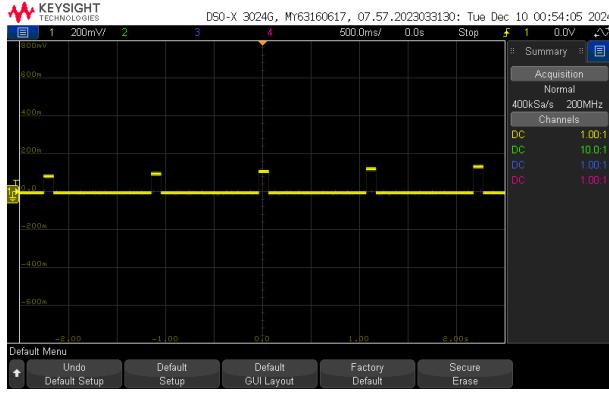


Figure 15: Voltage Measured at the Source of the NMOS

Figure 14 shows the output as read at the output of the DAC during the measurement cycle as verification of proper voltage control by the microcontroller. Figure 15 shows the voltage at the source of the NMOS transistor during the measurement cycle which verifies the proper switching of the MOSFET.

3.1.4 Current Measurement

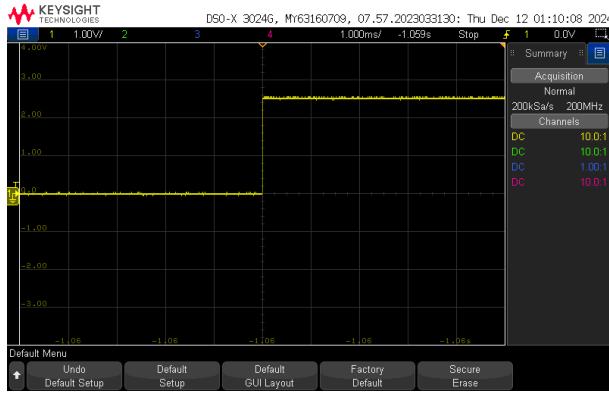


Figure 16: Voltage Measurement at the end of the Measurement Cycle Using a 9V Power Supply and 10Ω Sense Resistor

By measuring the voltage across the sense resistor during measurement, proper maximum current through the circuit can be verified. The voltage measurement from Figure 16 is the voltage during the final increment of the measurement step with a 9V power supply and a 10Ω sense resistor. The 2.5V measured together with the sense resistor corresponds to an expected 250mA.

3.1.5 Final Results

The following are the results on a scatter plot from measurements taken using the shield with an Arduino and the code from Appendix A:

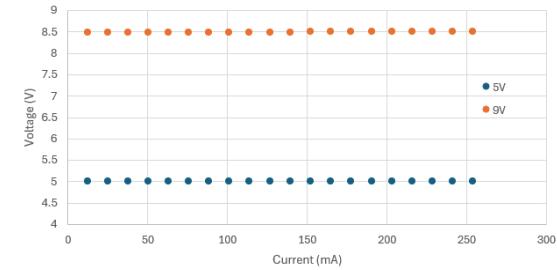


Figure 17: Thevenin Voltages from 5V (Blue) and 9V (Orange) Wall Wart Power Supplies and a 10Ω Sense Resistor

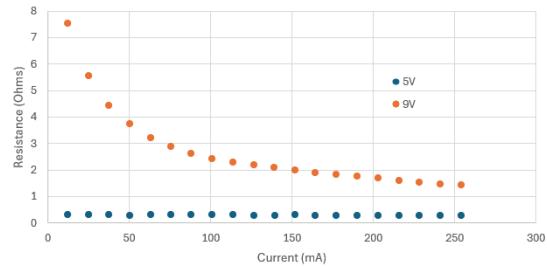


Figure 18: Thevenin Resistances from 5V (Blue) and 9V (Orange) Wall Wart Power Supplies and a 10Ω Sense Resistor

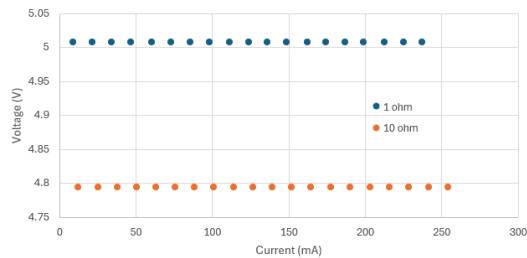


Figure 19: Thevenin Voltages from a Variable Power Supply at 5V Using 1Ω (Blue) and 10Ω (Orange) Sense Resistor

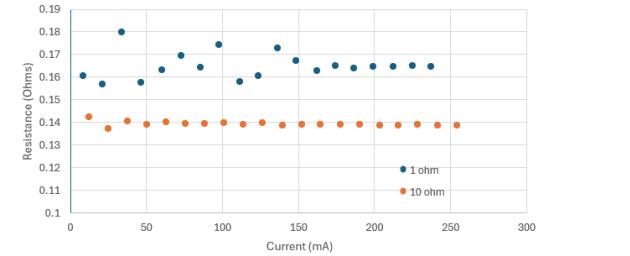


Figure 20: Thevenin Resistances from a Variable Power Supply at 5V Using 1Ω (Blue) and 10Ω (Orange) Sense Resistor

I first took measurements using the barrel jack using 5V and 9V wall warts. The Thevenin voltages and resistances output by the code are compiled on the scatter plots from Figures 17 and 18 respectively. These measurements were used to verify proper characterization of power supplies at different voltages using the barrel jack and the 10Ω resistor. I next verified the operation of the block terminal and 1Ω sense resistor using a variable DC power supply. Figure 19 shows the Thevenin Voltage results from the block terminal using both sense resistors and Figure 20 shows the Thevenin resistance results. These measurements are also used to verify proper operation of the ADC.

3.2 What Worked

By the metrics provided in the engineering specifications my board "worked". Both the barrel jack and block terminal were able to supply power for measurements, the header pins were in the correct positions, and the DAC, ADC, and MOSFET were all operational. Mounting some of the parts on the bottom side of the board allowed for the size of the board to easily be constrained to the area of the Arduino header pins.

3.3 What Didn't Work

I blew out the 1Ω resistor during tested when I forgot to switch the shorting flag I could implement some indication of which sense resistor is in operation using an additional smart LED and digital pin. I also mistakenly used a 2-pin header footprint in place of a block terminal. The block terminal was still able to be added with some bending of pins but the 1-pin header for the power supply switch ended up very close to the terminal making it difficult to operate.

4 Final Remarks

4.1 Things I Would Do Differently

- Place the switch for power supply selection further from the block terminal to make it easier to operate.
- Add some indication of the expected sense resistor.

4.2 Lessons Learned

- Pay close attention to the footprints used during design and their physical size in comparison to nearby parts.
- Adding additional indicators can help prevent the damage of power sensitive parts

Appendix A Code

```
1 #include <Wire.h>
2 #include <Adafruit_MCP4725.h>
3 #include <Adafruit_ADS1115.h>
4 #include <Adafruit_NeoPixel.h>
5
6 #define LED_PIN 6
7 #define MPU_LEDS 3
8
9 Adafruit_NeoPixel strip(NEP_LEDs, LED_PIN, NEO_GRB + NEO_KHZ800);
10
11 Adafruit_ADS1115 ads;
12 Adafruit_MCP4725 dac;
13
14 float R_sense = 10.0; //current sense
15 float V_VIN = 5.0; //VIN voltage for taking measurements
16 long ttimeoff_msec = 1000000; // time to cool off
17 int tcounter_off = 0; // counter for number of samples off
18
19 float v_divider = 5000.0 / 10000.0; //voltage divider on the VIN
20 float DAC_ADU_per_v = 4095.0 / 5.0; //conversion from volts to ADU
21
22 float I_mA; //the current we want to output, in mA
23 float I_A = 0.0; //the current we want to output, in amps
24 long tloop_stop_msec = 1000000; //stop time for each loop
25 float V_VIN_on_V1; // the value of the VVIN voltage
26 float V_VIN_off_V1; // the value of the VVIN voltage
27 float R_sense_mA; // the value of the sense resistor
28 float I_sense_off_A1; // the current through the sense resistor
29 float I_max_A = 0.250; // was current to set for
30 int npnts = 100; //number of points to measure
```

```
31 float I_stop_A = I_max_A / npnts; //stop current change
32 float I_mA; //the current measured current load
33 float V_VIN_Thevinin_V1;
34 float V_VIN_loaded_V1;
35 float R_thevenin;
36 float I_g;
37
38 uint8_t strip_interpolate(uint8_t r1, uint8_t g1, uint8_t b1, uint8_t r2, uint8_t g2, uint8_t b2, float fraction) {
39     uint8_t r = r1 + (r2 - r1) * fraction;
40     uint8_t g = g1 + (g2 - g1) * fraction;
41     uint8_t b = b1 + (b2 - b1) * fraction;
42     return strip.color(r, g, b);
43 }
44
45 void turnOffLEDs() {
46     for (int i = 0; i < strip.numPixels(); i++) {
47         | strip.setPixelColor(i, 0); // set the color of each LED to black (off)
48     }
49     strip.show(); // apply the changes
50 }
51
52 void setup() {
53     Serial.begin(115200);
54     dac.begin(0x00); //set address in either 0x00, 0x01, 0x02, 0x03, 0x04 or 0x05
55     ads.begin(0x40); //set address to 0x40; //sets the output current to 0 initially
56     // ads.setGain(GAIN_TWOTHIRDS);
57     // 2/3x gain +/- 0.140V 1 bit = 3mV 0.1875mV (default)
58     // ads.setGain(GAIN_TWOFIFTHS); // 5/6x gain +/- 0.280V 1 bit = 6mV 0.3750mV
59     // ads.setGain(GAIN_FOURTHS); // 7/8x gain +/- 0.420V 1 bit = 12mV 0.6250mV
60     // ads.setGain(GAIN_EIGHTHS); // 15/16x gain +/- 0.560V 1 bit = 30mV 0.9375mV
```

```

56 // ads.setGain(GAIN_EIGHT); // 0x gain = 0x200 * 1 bit = 0.125W 0.0078125W
57 // ads.setGain(GAIN_SIXTEEN); // 0x gain = 0x250 * 1 bit = 0.125W 0.0078125W
58 ads.begin(); // note - you can put the address of the ADS111 here if needed
59 ads.setClockRate(MASTER_ADS111S_800SPS); // sets the ADS111S for higher speed
60
61 //I2C code
62 strip.begin(); // Initialize the NeoPixel strip
63 strip.setBrightness(0);
64 strip.show(); // ensure all LEDs are off initially
65
66
67 void loop() {
68     uint8_t r1, g1, b1, b2, r2, g2, b2;
69     float v, v_min, v_max;
70     for (i = 1; i < npts; i++) {
71         I_A = i / t_step_A;
72         if (I_A > 1) I_A = 1;
73         func.setOff();
74         func.setVoff(v);
75         strip.setBrightness(0);
76         strip.show();
77         func.setOff();
78         func.setVoff(v);
79         strip.setBrightness(0);
80         strip.show();
81         I_A.load_A = I_A.sense_on_A - I_A.sense_off_A; //load current
82         V_VTH_thevenin_v = V_VTH.off.v;
83         V_VTH_thevenin_v = V_VTH.loaded_v - V_VTH.thevenin_v;
84         if (V_VTH.loaded_v < 0.75 * V_VTH.thevenin_v) i = npts; //stops the ramping
85         Serial.print("i = ");
86         Serial.print(i);
87         Serial.print(" V_VTH.loaded_v = ");
88         Serial.print(V_VTH.loaded_v);
89         Serial.print(" V_VTH.thevenin_v = ");
90         Serial.print(V_VTH.thevenin_v);
91         Serial.print(" I_A = ");
92         Serial.print(I_A);
93         Serial.print(" V_VTH.loaded_v = ");
94         Serial.print(V_VTH.loaded_v);
95         Serial.println(" V_VTH.thevenin_v = ");
96         if (i < 10) {
97             // Red to Yellow transition
98             r1 = 255; g1 = 0; b1 = 0; // Red
99             r2 = 255; g2 = 255; b2 = 0; // Yellow
100            fraction = 1 / 10.0; // fraction for this step
101        } else {
102            // Yellow to Green Transition
103            r1 = 255; g1 = 255; b1 = 0; // Yellow
104            r2 = 0; g2 = 255; b2 = 0; // Green
105            fraction = (i - 10) / 10.0; // fraction for this step
106        }
107        uint32_t color = interpolateColor(r1, g1, b1, r2, g2, b2, fraction);
108        // set all LEDs to this color
109        for (int j = 0; j < MMLEDS; j++) {
110            strip.setPixelColor(j, color);
111        }
112        strip.show();
113    }
114    Serial.println("done");
115    tone(t2, 500);
116    tone(t2, 500);
117    tone(t2, 500);
118    delay(500);
119    noTone(t2);
120    delay(5000);

```



```

121
122 void func.setOff() {
123     ads.setVoltageOn(false); //sets the output current
124     icounter_off = 0; //starting the current counter
125     V_VTH.off.v = 0; //initializes the VTH voltage average
126     I_A.off.v = 0; //initializes the current average
127     itime_stop_usc = micros() + itime_off_usc * 1000; // stop time
128     while (micros() < itime_stop_usc) {
129         I_A.off.v = ads.readADC_differential_0_1() * ADC_V_per_ADU / v.divider + V_VTH.off.v;
130         I_A.sense_off_A = ads.readADC_differential_2_3() * ADC_V_per_ADU / R_sense + I_A.sense_off_A; icounter_off++;
131         V_VTH.off.v = V_VTH.off.v / icounter_off;
132         I_A.sense_on_A = I_A.sense_off_A / icounter_off;
133     }
134 }
135 void func.setOn() {
136     I_A.MC_ADU = 1.0 * R_sense * DAC_ADU_per_V;
137     ads.setVoltageOn(true); //sets the output current
138     icounter_on = 0; //starting the current counter
139     V_VTH.on.v = 0.0; //initialize the VTH voltage average
140     I_A.sense_on_A = 0.0; // initialize the current average
141     itime_stop_usc = micros() + itime_stop_usc * 1000; // stop time
142     while (micros() < itime_stop_usc) {
143         I_A.V_VTH_on.v = ads.readADC_differential_0_1() * ADC_V_per_ADU / v.divider + V_VTH.on.v;
144         I_A.sense_on_A = ads.readADC_differential_2_3() * ADC_V_per_ADU / R_sense +
145         I_A.sense_on_A; icounter_on;
146     }
147     dac.setVoltageOn(true); //sets the output current to zero
148     I_A.sense_on_A = I_A.sense_on_A / icounter_on;
149     I_A.sense_on_A = I_A.sense_on_A / icounter_on;
150 }

```